

Universidade do Minho
Escola de Engenharia

Fábio Oliveira, PG50363
Vitor Ferreira, PG50802

8051 Microcontroller - FPGA Implementation

Master's in Industrial Electronics and Computers
Engineering

Embedded Systems

Professor:
Adriano Tavares

January, 2022

List of Figures

1	8051 Architecture	2
2	Memory organization	2
3	On-chip data Memory	3
4	Full circuit	8
5	Program Counter diagram	9
6	Instruction Register diagram	10
7	Accumulator diagram	11
8	PSW diagram	12
9	ALU diagram	12
10	state diagram control unit	13
11	execute state for each instruction	14
12	RAM diagram	16
13	Register Bank	17
14	ROM diagram	18
15	TIMER0 diagram	19
16	Interrupt Controller diagram	20
17	Simulation Waveform	22
18	Simulation Waveform	23
19	Simulation Waveform	23
20	Simulation Waveform	24
21	Simulation Waveform	25
22	Simulation Waveform	25
23	Simulation Waveform	26
24	Simulation Waveform	27
25	Simulation Waveform	27
26	Simulation Waveform	28
27	Simulation Waveform	29
28	Simulation Waveform	29
29	Simulation Waveform	30
30	Simulation Waveform	30
31	Simulation Waveform	31

List of Tables

1	Mapping of states to control signals	15
---	--	----

Contents

1	Introduction	1
1.1	Requirements	1
2	8051 Architecture Overview	1
2.1	Overview of 8051 Microcontroller	1
2.2	On-Chip Memory Organization	1
3	Instruction Set	4
3.1	Data Transfer Instructions	4
3.1.1	MOV Rn, #immediate	4
3.1.2	MOV A, Rn	4
3.1.3	MOV direct, Rn	4
3.1.4	MOV Rn, A	4
3.1.5	MOV A, #immediate	5
3.1.6	MOV A, direct	5
3.1.7	MOV direct, A	5
3.2	Arithmetic and Logical Instructions	5
3.2.1	ADD A, #immediate	5
3.2.2	SUBB A, #immediate	6
3.2.3	ORL A, #immediate	6
3.2.4	ANL A, #immediate	6
3.2.5	XRL A, #immediate	6
3.3	Branch Instructions	6
3.3.1	SJMP offset	6
3.3.2	JNZ offset	7
3.3.3	JZ offset	7
3.3.4	JNC offset	7
3.3.5	RETI	7
4	Verilog Implementation	8
4.1	General Overview	8
4.2	Datapath	8
4.2.1	Program Counter	9
4.2.2	Instruction Register	10
4.2.3	Accumulator	11
4.2.4	Program Status Word	11
4.2.5	Arithmetic Logic Unit	12
4.3	Control Unit	13
4.3.1	State Machine	13

4.4	RAM	15
4.4.1	Register Bank	16
4.5	ROM	17
4.6	Timer 0	18
4.7	Interrupt Controller	19
4.8	Constraints	20
5	Verification and validation	22
5.1	Arithmetic, Logic and Data Transfer Instructions	22
5.1.1	ADD A, immediate	22
5.1.2	SUBB A, immediate	22
5.1.3	ORL A, immediate	23
5.1.4	ANL A, immediate	24
5.1.5	XRL A, immediate	24
5.2	Branch Instructions	25
5.2.1	JNC	25
5.2.2	JNZ	26
5.2.3	JZ	28
5.3	Timer 0	29
5.3.1	Mode 1 - 16-bit timer	29
5.3.2	Mode 2 - 8-bit auto reload timer	29
5.4	Interrupts	30
5.4.1	Timer 0	30
5.4.2	External Interrupt 0	30
5.5	Test in Hardware	31
A	Verilog module code	33
A.1	Datapath	33
A.1.1	Program counter	35
A.1.2	Instruction Register	36
A.1.3	Accumulator	37
A.1.4	Program Status Word	38
A.1.5	Arithmetic Logic Unit	39
A.2	Control Unit	40
A.3	RAM	46
A.4	ROM	48
A.5	Timer 0	49
A.6	Interrupt Controller	51

1 Introduction

The objective of this project is to design an 8051 microcontroller, model and simulate it using the Verilog hardware description language, and finally to implement it in hardware using a programmable field gate array(FPGA). This document describes the microcontroller design, the test code used to verify it, and the physical hardware implementation.

1.1 Requirements

The following are the requirements for this project:

- Implement a subset of the 8051 Instruction Set.
- Use fixed length instructions
- Implement a timer peripheral
- Implement two interrupts

2 8051 Architecture Overview

2.1 Overview of 8051 Microcontroller

The 8051 Microcontroller is one of the basic types of microcontrollers, designed by Intel in 1980s. This microcontroller is based on Harvard Architecture, meaning that the program and data memory spaces are separated. It has a total of 128 bytes of on-chip RAM, 4KB of on-chip ROM, and a variety of peripheral interfaces including serial communication, timers, and interrupt controller, also has a variety of instruction set, including arithmetic, logical, branching, and data transfer instructions, making it suitable for a wide range of applications.

2.2 On-Chip Memory Organization

The 8051 microcontroller has a variety of memory types that can be used for different purposes, including program memory, data memory, and special function registers. These memory types are used to store the program instructions, data used by the program, and configuration settings for the microcontroller. With a combination of internal and external memory, the 8051 can support programs of varying size and complexity.

2.2 ON-CHIP MEMORY ORGANIZATION

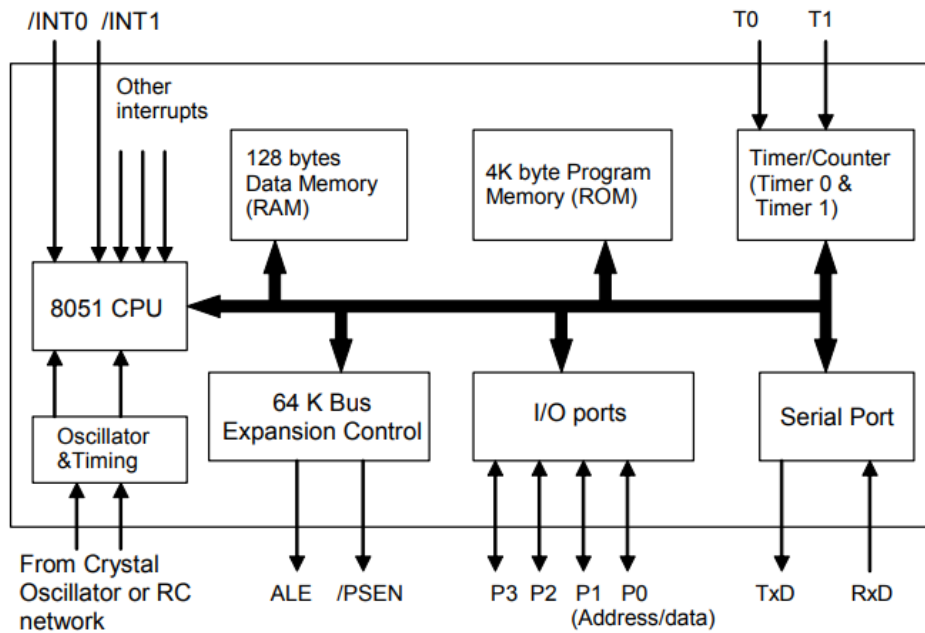


Figure 1: 8051 Architecture

Understanding the 8051 On-Chip Memory Organization is essential for effective and efficient programming of the 8051 microcontroller.

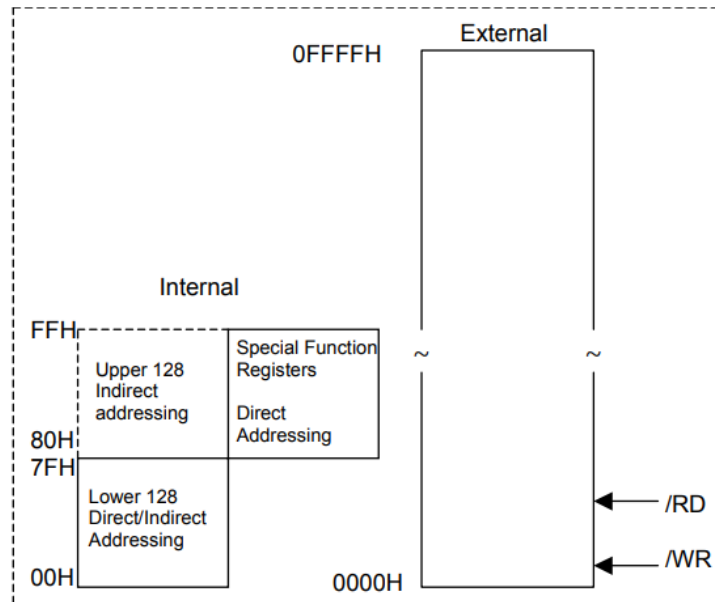


Figure 2: Memory organization

2.2 ON-CHIP MEMORY ORGANIZATION

With both internal and external data memory, which is depicted in Figure 2. The internal data memory is further divided into three sections: Lower 128, Upper 128, and SFR. These sections have 384 physical bytes of memory space, with the Upper 128 and SFR sharing the same addresses from location 80H to FFH. The internal data memory is a Read/Write or Random Access Memory, and Figures 3a and 3b provide more detailed information about it. Instructions using direct or indirect addressing modes can be used to access the different memory blocks as required.

Byte Address	Bit Address								
FF									
F0	F7	F6	F5	F4	F3	F2	F1	F0	B
E0	E7	E6	E5	E4	E3	E2	E1	E0	ACC
D0	D7	D6	D5	D4	D3	D2	-	D0	PSW
B8	-	-	-	BC	BB	BA	B9	B8	IP
B0	B7	B6	B5	B4	B3	B2	B1	B0	P3
A8	AF	-	-	AC	AB	AA	A9	A8	IE
A0	A7	A6	A5	A4	A3	A2	A1	A0	P2
99	Not bit-addressable								SBUF
98	9F	96	95	94	93	92	91	90	SCON
90	97	96	95	94	93	92	91	90	P1
8D	Not bit-addressable								TH1
8C	Not bit-addressable								TH0
8B	Not bit-addressable								TL1
8A	Not bit-addressable								TL0
89	Not bit-addressable								TMOD
88	8F	8E	8D	8C	8B	8A	89	88	TCON
87	Not bit-addressable								PCON
83	Not bit-addressable								DPH
82	Not bit-addressable								DPL
81	Not bit-addressable								SP
80	87	86	85	84	83	82	81	80	P0

Byte Address	Bit Address								
7F									
	General Purpose RAM								
30									
2F	7F	7E	7D	7C	7B	7A	79	78	B i t A d d r e s s a b l e
2E	77	76	75	74	73	72	71	70	
2D	6F	6E	6D	6C	6B	6A	69	68	
2C	67	66	65	64	63	62	61	60	
2B	5F	5E	5D	5C	5B	5A	59	58	
2A	57	56	55	54	53	52	51	50	
29	4F	4E	4D	4C	4B	4A	49	48	
28	47	46	45	44	43	42	41	40	
27	3F	3E	3D	3C	3B	3A	39	38	
26	37	36	35	34	33	32	31	30	
25	2F	2E	2D	2C	2B	2A	29	28	
24	27	26	25	24	23	22	21	20	
23	1F	1E	1D	1C	1B	1A	19	18	
22	17	16	15	14	13	12	11	10	
21	0F	0E	0D	0C	0B	0A	09	08	
20	07	06	05	04	03	02	01	00	
1F	Bank 3								
18									
17	Bank 2								
10									
0F	Bank 1								
08									
07	Default Register Bank for R0 – R7								
00									

(a) SFR

(b) Register Banks and RAM

Figure 3: On-chip data Memory

3 Instruction Set

This section briefly describes each of the instructions implemented. The instructions chosen have all a fixed size of two bytes, in order to simplify the implementation. Operations are considered to be 8-bit operations with 8-bit results.

3.1 Data Transfer Instructions

3.1.1 MOV Rn, #immediate

This instruction moves an 8-bit immediate value to a register. The format of the instruction is MOV Rn, #immediate. Here Rn refers to the register where the value will be stored and immediate is the immediate value to be stored in the register.

Encoding

01111nnn	immediate
----------	-----------

3.1.2 MOV A, Rn

This instruction moves the contents of a register to the accumulator. The format of the instruction is MOV A, Rn. Here A refers to the accumulator and Rn refers to the register containing the data.

Encoding

11101nnn	00000000
----------	----------

3.1.3 MOV direct, Rn

This instruction transfers the contents of register Rn to a direct address specified by the 8-bit operand. The operand acts as the memory address where the contents of Rn will be stored.

Encoding

10001nnn	direct
----------	--------

3.1.4 MOV Rn, A

This instruction transfers the content of the accumulator to a register. The format of the instruction is MOV Rn, A. Here Rn refers to the register where the value will be stored and A is the accumulator.

Encoding

1111nnn	00000000
---------	----------

3.1.5 MOV A, #immediate

This instruction moves an 8-bit immediate value to the accumulator. The format of the instruction is MOV A, #immediate. Here A refers to the accumulator where the value will be stored and immediate is the immediate value to be stored in the register.

Encoding

01110100	immediate
----------	-----------

3.1.6 MOV A, direct

This instruction is used to move the contents of a specified direct address in memory to the accumulator register A.

Encoding

11100101	direct
----------	--------

3.1.7 MOV direct, A

This instruction is used to transfer the contents of accumulator to a direct address. The direct address is specified in the lower 8-bits of the instruction. The 8-bit data stored in the accumulator is copied to the specified direct address.

Encoding

11110101	direct
----------	--------

3.2 Arithmetic and Logical Instructions

3.2.1 ADD A, #immediate

This instruction adds an immediate value to the contents of the accumulator. The immediate is specified in the lower 8-bits of the instruction.

Encoding

00100100	immediate
----------	-----------

3.2.2 SUBB A, #immediate

This instruction subtracts an immediate value to the contents of the accumulator. The immediate is specified in the lower 8-bits of the instruction.

Encoding

10010100	immediate
----------	-----------

3.2.3 ORL A, #immediate

This instruction performs a bitwise OR operation between the accumulator and an immediate value, and stores the result back in the accumulator.

Encoding

01000100	immediate
----------	-----------

3.2.4 ANL A, #immediate

This instruction performs a bitwise AND operation between the accumulator and an immediate value, and stores the result back in the accumulator.

Encoding

01010100	immediate
----------	-----------

3.2.5 XRL A, #immediate

This instruction performs a bitwise XOR operation between the accumulator and an immediate value, and stores the result back in the accumulator.

Encoding

01100100	immediate
----------	-----------

3.3 Branch Instructions**3.3.1 SJMP offset**

This instruction transfers execution to the specified address. The address is calculated by adding the signed relative offset in the second byte of the instruction to the address of the following instruction. The range of destination addresses is from 128 before the next instruction to 127 bytes after the next instruction.

Encoding

10000000	offset
----------	--------

3.3.2 JNZ offset

This instruction transfers control to the specified address if the value in the accumulator is not 0. If the accumulator has a value of 0, the next instruction is executed.

Encoding

01110000	offset
----------	--------

3.3.3 JZ offset

The JZ instruction transfers control to the specified address if the value in the accumulator is 0. Otherwise, the next instruction is executed.

Encoding

01100000	offset
----------	--------

3.3.4 JNC offset

This instruction transfers program control to the specified address if the carry flag is 0.

Encoding

10100000	offset
----------	--------

3.3.5 RETI

The RETI instruction is used to end an interrupt service routine. This instruction pops the high-order and low-order bytes of the PC (and decrements the stack pointer by 2) and restores the interrupt logic to accept additional interrupts. No other registers are affected by this instruction.

Encoding

00110010	00000000
----------	----------

4 Verilog Implementation

4.1 General Overview

In figure 4 is presented the full microcontroller implementation with all the modules used.

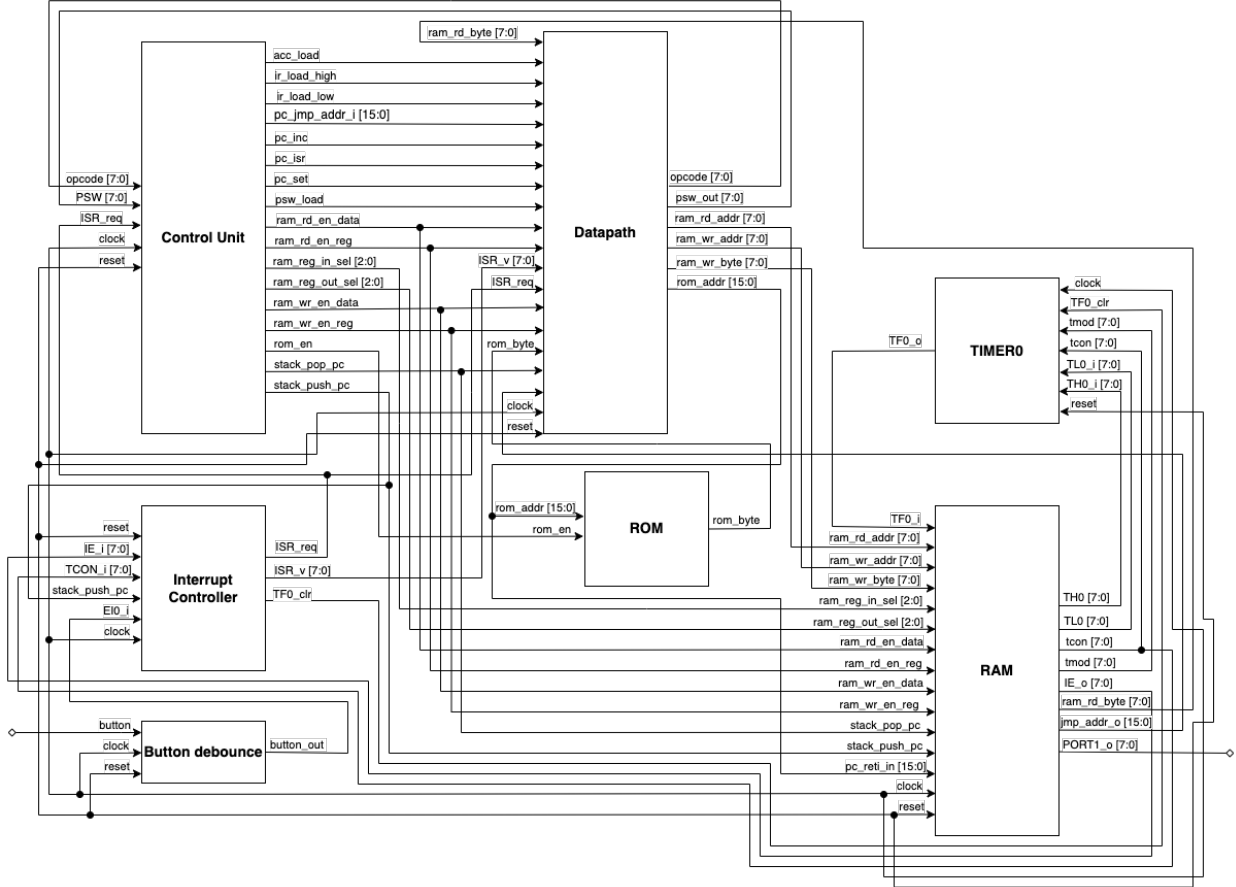


Figure 4: Full circuit

4.2 Datapath

The datapath is responsible for performing data processing operations and, in the implementation made, it consists of multiple components, such as program counter, instruction register, arithmetic logic unit, accumulator, and psw. These components are interconnected and interact with each other to perform various tasks.

The module code is shown in Appendix A.1.

4.2.1 Program Counter

The program counter, presented in figure 5, holds the address of the next instruction byte and is used to index ROM when fetching instructions, due to this fact the width of the program counter is 16 bits.

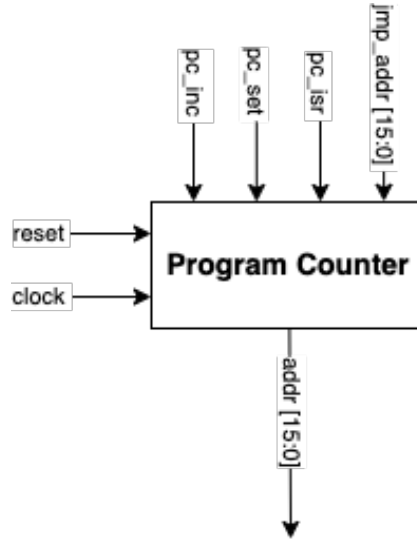


Figure 5: Program Counter diagram

The program counter has the following inputs:

- **pc_inc** : an increment signal that increments the program counter by one.
- **pc_set** : a set signal that sets the program counter to a specific value specified by the jmp_addr input.
- **pc_isr** : an interrupt signal that indicates the need to jump to an interrupt service routine vector.
- **jmp_addr** : a 16-bit input that specifies the address to which the program counter should be set.

The program counter has a single output, addr, which is a 16-bit register that holds the current value of the program counter.

On the rising edge of the clock, the value of addr is updated based on the values of the inputs. If the reset input is asserted, the program counter is set to 0. If the pc_inc input is asserted, the program counter is incremented by 1. If the pc_set input is asserted, the program counter is offset to the value

of `jmp_addr`. If the `pc_isr` input is asserted, the program counter is set to the value of `jmp_addr`.

The module code is shown in Appendix A.1.1.

4.2.2 Instruction Register

The instruction register, presented in figure 6, holds the instruction to be executed, as the chosen width of the instructions is 16 bits the instruction register is 16 bits wide.

 


Figure 6: Instruction Register diagram

When the `reset` signal is high, the IR register is set to zero. When the `clock` signal goes high, the values of `ir_load_high` and `ir_load_low` control signals are checked. If `ir_load_high` is high, the 8 most significant bits of IR are updated with the value of `rom_byte`. If `ir_load_low` is high, the 8 least significant bits of IR are updated with the value of `rom_byte`. The IR register holds the instruction until the next clock cycle and acts as a temporary storage for the instruction.

The module code is shown in Appendix A.1.2.

4.2.3 Accumulator

The Accumulator, present in figure 7, is used for arithmetic and logic operations.

When reset is high the accumulator is set to zero. The data_in input signal provides the data that is to be stored in the accumulator, and, the write_en input signal, when high, enables writing to the accumulator.

 


Figure 7: Accumulator diagram

The module code is shown in Appendix A.1.3.

4.2.4 Program Status Word

The Program Status Word (PSW), presented in figure 8, contains status bits that reflect the current CPU state.

The PSW register is updated on every positive edge of the clock signal. If the reset signal is high, the PSW register is set to zero. If the write_en signal is high, the PSW register is updated with the values of the carry, auxiliary carry, overflow, zero, and parity flags provided by the ALU.

 


Figure 8: PSW diagram

The module code is shown in Appendix A.1.4.

4.2.5 Arithmetic Logic Unit

The ALU, presented in figure 9, consists entirely of combinational logic, and operations are performed whenever the inputs change. The operations are performed based on the opcode of the instruction, as the instruction set chosen always uses the accumulator as a source of the operations the output of the accumulator is connected directly to operand1. As the output of the ALU is connected to the accumulator the MOV instructions to the accumulator are also implemented on the ALU. If the result is all zeros, the psw_z bit is set. Likewise, the parity flag, psw_p, is set whenever the result is odd. The carry flag, psw_c, is set when the ninth bit of the result is 1.

 


Figure 9: ALU diagram

The module code is shown in Appendix A.1.5.

4.3 Control Unit

4.3.1 State Machine

The state machine is responsible for decoding the instruction opcode and activate the corresponding control signals for all the other modules. The state diagram for the state machine is shown in figure 10

 


Figure 10: state diagram control unit

In order to simplify the state machine the state diagram above was presented, but in reality each instruction has a own state for **s_execute** as presented in figure 11.

Below is presented the function of each state.

- **s_start**: initial state
- **s_fetch_1**: state to fetch the most significant byte of the instruction to be executed
- **s_fetch_2**: state to fetch the least significant byte of the instruction to be executed
- **s_decode**: state to decode the opcode

 


Figure 11: execute state for each instruction

- **s_mov_ri**: state to execute the instruction MOV Rn, #immediate
- **s_mov_dr**: state to execute the instruction MOV direct, Rn
- **s_mov_ad**: state to execute the instruction MOV A, direct
- **s_mov_ra**: state to execute the instruction MOV Rn, A
- **s_mov_ai**: state to execute the instruction MOV A, #immediate
- **s_mov_ar**: state to execute the instruction MOV A, Rn
- **s_mov_da**: state to execute the instruction MOV direct, A
- **s_add_ai**: state to execute the instruction ADD A, #immediate
- **s_subb_ai**: state to execute the instruction SUBB A, #immediate
- **s_orl_ai**: state to execute the instruction ORL A, #immediate
- **s_anl_ai**: state to execute the instruction ANL A, #immediate
- **s_xrl_ai**: state to execute the instruction XRL A, #immediate
- **s_sjmp**: state to execute the instruction SJMP offset
- **s_jnz**: state to execute the instruction JNZ offset

- **s_jz**: state to execute the instruction JZ offset
- **s_jnc**: state to execute the instruction JNC offset
- **s_reti**: state to execute the instruction RETI

The table 1 represents the mapping of the states to control signals.

	ram_rd_en_reg	ram_wr_en_reg	ram_rd_en_data	ram_wr_en_data	rom_en	pc_inc	pc_set	pc_isr	ir_load_high	ir_load_low	acc_load	stack_push_pc	stack_pop_pc	psw_load
Start	0	0	0	0	0	0	0	ISR_req	0	0	0	ISR_req	0	0
Fetch_1	0	0	0	0	1	1	0	0	1	0	0	0	0	0
Fetch_2	0	0	0	0	1	1	0	0	0	1	0	0	0	0
Decode	0	0	0	0	0	0	0	0	0	0	0	0	0	0
MOV_RI	0	1	0	0	0	0	0	0	0	0	0	0	0	0
MOV_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	0
MOV_AR	1	0	0	0	0	0	0	0	0	0	1	0	0	0
MOV_RA	0	1	0	0	0	0	0	0	0	0	0	0	0	0
MOV_AD	0	0	1	0	0	0	0	0	0	0	1	0	0	0
MOV_DR	1	0	0	1	0	0	0	0	0	0	0	0	0	0
MOV_DA	0	0	0	1	0	0	0	0	0	0	0	0	0	0
ADD_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	1
SUBB_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	1
ORL_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	1
ANL_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	1
XRL_AI	0	0	0	0	0	0	0	0	0	0	1	0	0	1
JNZ	0	0	0	0	0	0	~PSW[1]	0	0	0	0	0	0	0
JZ	0	0	0	0	0	0	PSW[1]	0	0	0	0	0	0	0
SJMP	0	0	0	0	0	0	1	0	0	0	0	0	0	0
JNC	0	0	0	0	0	0	~PSW[7]	0	0	0	0	0	0	0
RETI	0	0	0	0	0	0	0	1	0	0	0	0	1	0

Table 1: Mapping of states to control signals

The module code is shown in Appendix A.2.

4.4 RAM

The RAM, presented in figure 12, has inputs to read and write enable signals for both the register bank and the data memory, the select signals for both reading and writing from the register bank, the read and write addresses for the data memory, the byte being written to the memory, signals to push or pop the program counter onto or from the stack, input signal for the

timer 0 overflow flag and the program counter to load to the stack, it also has outputs for the read data from the data memory, the program counter address stored on the stack and several memory-mapped register values such as Timer Control Register (TCON), Timer Mode Register (TMOD), Timer 0 Low Byte (TL0) and Timer 0 High Byte (TH0), the Interrupt Enable register (IE) and P1 (PORT1).

When the either of the write enable signals are high, the data present in `ram_wr_byte` is store either on the registers or on the address specified by `ram_wr_addr`.

If the `stack_push_pc` signal is high, the current program counter is pushed onto the stack and the stack pointer is incremented by 2. If the `stack_pop_pc` signal is high, the stack pointer is decremented by 2, and the jump address (PC) from the stack is outputted.

The output `ram_rd_byte` is assigned the value of the data memory at the read address specified by `ram_rd_addr`, if the read enable signals are high. The `jmp_addr_o` output is assigned the address from the stack if the `stack_pop_pc` signal is high.

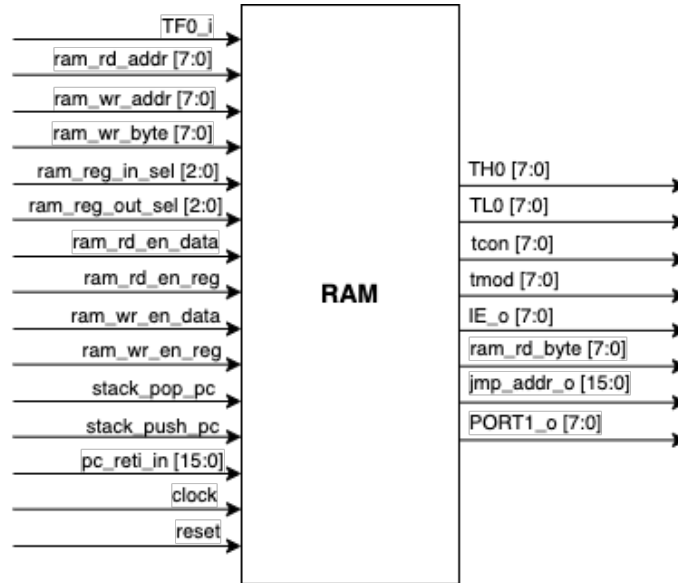


Figure 12: RAM diagram

The module code is shown in Appendix A.3.

4.4.1 Register Bank

The register bank, presented in 13, contains 8 registers each one 8-bits wide.

When the `write_en` signal, connected to `ram_wr_en_reg`, is high the contents of `reg_in_data` are stored to the register selected by `reg_in_select`. Otherwise, when the `read_en` signal, connected to `ram_rd_en_reg`, is high the contents of the register selected is passed to `reg_data_out`.

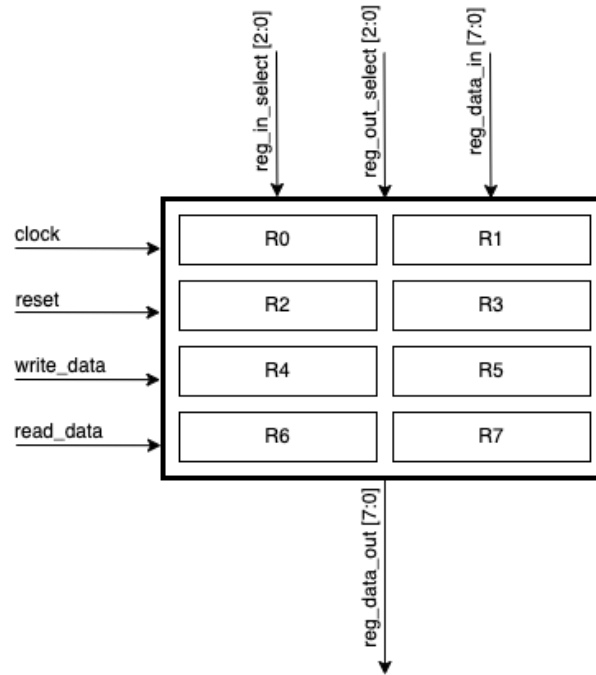


Figure 13: Register Bank

4.5 ROM

The ROM, presented in figure 14 is used to store the program code for a microcontroller. The size defined for the ROM is 256 words of 8 bits each, but it is possible to have 64kb of memory. The inputs to the module are a reset signal, enable signal (`rom_en`), address (`rom_addr`), and the output is the byte stored at that address (`rom_byte`).

 


Figure 14: ROM diagram

4.6 Timer 0

The block diagram for the timer 0 is presented in figure 15, the 8051 timer 0 has various modes of operation:

- **Mode 0 (13-bit Timer mode):** In this mode, the timer increments every machine cycle and the overflow flag is set when the timer overflows from 8192 to 0.
- **Mode 1 (16-bit Timer mode):** In this mode, the timer is incremented every machine cycle and the overflow flag is set when the timer overflows from 65536 to 0.
- **Mode 2 (8-bit Auto-Reload mode):** In this mode, the timer is incremented every machine cycle. When the timer overflows from 255 to 0, the timer is automatically reloaded with a value stored in the reload register.
- **Mode 3 (Split Timer mode):** In this mode, Timer 0 is split into two 8-bit timers, Timer 0 and Timer 1. Both timers can operate independently and can be set up for different modes of operation.

As the most used modes are mode 1 and 2 these were the only modes implemented.

The Timer 0 takes several inputs such as a clock signal, a reset signal, tmod and tcon which control the mode of operation, TH0_i and TL0_i which are used to load the initial value of the timer, TF0_clr which is used to clear the timer overflow flag and an output signal TF0_o which indicates if the timer has overflowed.

 


Figure 15: TIMER0 diagram

4.7 Interrupt Controller

The block diagram for the interrupt controller is presented in figure 16. The interrupt controller has inputs for the clock signal, reset signal, stack_push_pc signal in order to know when the interrupt is attended, as well as input signals for the Interrupt Enable (IE_i) register, the Timer Control (TCON_i) register, and the external interrupt 0 (EI0_i). It also has several outputs including the signal to clear the Timer 0 overflow flag (TF0_clr), the Interrupt Service Routine (ISR_v) address, and the Interrupt Service Request (ISR_req) signal.

The interrupt controller's main function is to generate the ISR_req signal when an interrupt occurs. This is done by checking the values of the input signals and the current state of the ISR_req signal. If the external interrupt 0 (EI0_i) is set, the Interrupt Enable bit for External Interrupt 0 (IE_i[0]), and the global Interrupt Enable bit (IE_i[7]) are set, and there is not already an ISR_req signal, the ISR_req signal will be set and the ISR_v register will be loaded with the address of the External Interrupt 0.

Similarly, if the Timer 0 Interrupt flag (TCON_i[5]) is set, the Interrupt Enable bit for Timer 0 (IE_i[1]), and the global Interrupt Enable bit (IE_i[7]) are set, and there is not already an ISR_req signal, the ISR_req signal will be set and the ISR_v register will be loaded with the address of the Timer 0 ISR.

The ISR_req signal is cleared when the stack push PC signal is asserted, which means the interrupt has been serviced. The TF0_clr output is used to clear the Timer 0 interrupt flag and is set when the ISR_req signal is set.

In summary, the interrupt controller is responsible for generating the ISR_req signal and the ISR_v address when an interrupt occurs, and for clearing the interrupt flags and ISR_req signal when the interrupt has been serviced.

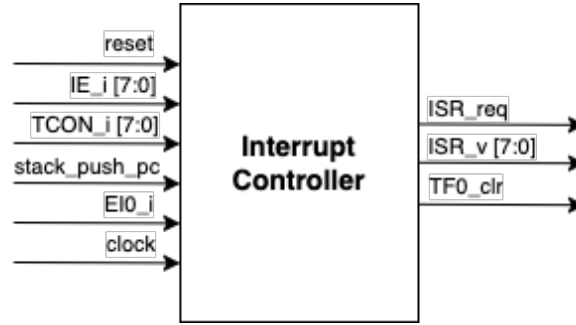


Figure 16: Interrupt Controller diagram

4.8 Constraints

The following constraints were used. The clock frequency is set to 50MHz, the reset input is set to the button Y16 and the external interrupt input is mapped to the K19 button. The I/O port P1 four least significant bits are set to the LED's and the rest is mapped to ports with pull-down.

```

1 set_property IOSTANDARD LVCMOS33 [get_ports reset]
2
3 set_property -dict {PACKAGE_PIN K17 IOSTANDARD LVCMOS33} [
  get_ports clock]
4 create_clock -period 20.000 -name sys_clk_pin -waveform
  {0.000 10.000} -add [get_ports clock]
5
6 set_property PACKAGE_PIN Y16 [get_ports reset]
7 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [7]}]
8 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [6]}]
9 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [5]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [4]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [3]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [2]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [1]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {PORT1_o [0]}]
15 set_property PACKAGE_PIN M14 [get_ports {PORT1_o [0]}]
16 set_property PACKAGE_PIN M15 [get_ports {PORT1_o [1]}]
17 set_property PACKAGE_PIN G14 [get_ports {PORT1_o [2]}]
18 set_property PACKAGE_PIN D18 [get_ports {PORT1_o [3]}]
19 set_property PACKAGE_PIN H15 [get_ports {PORT1_o [4]}]
20 set_property PACKAGE_PIN J15 [get_ports {PORT1_o [5]}]
21 set_property PACKAGE_PIN W16 [get_ports {PORT1_o [6]}]
22 set_property PACKAGE_PIN V12 [get_ports {PORT1_o [7]}]
23 set_property PULLDOWN true [get_ports {PORT1_o [7]}]
24 set_property PULLDOWN true [get_ports {PORT1_o [6]}]
25 set_property PULLDOWN true [get_ports {PORT1_o [5]}]
26 set_property PULLDOWN true [get_ports {PORT1_o [4]}]

```

```
27 set_property PACKAGE_PIN K19 [get_ports pb_1]
28 set_property IOSTANDARD LVCMOS33 [get_ports pb_1]
```

5 Verification and validation

5.1 Arithmetic, Logic and Data Transfer Instructions

5.1.1 ADD A, immediate

The following assembly code was tested.

```
1 MOV R5, #08h
2 MOV A, R5
3 ADD A, #11h
4 MOV 50h, A
```

 


Figure 17: Simulation Waveform

It is possible to see in figure 17 that the value 08H is being stored on R5 (simulation line 7), after that the value from R5 is being stored on the accumulator and later 11H is added to 08H equaling 19H, this value stored on the accumulator is then stored on position 50H of the RAM (simulation line 8). Moreover, the value on the PSW is updated on par with the result.

5.1.2 SUBB A, immediate

The following assembly code was tested.

```
1 MOV A, #10h
2 SUBB A, #20h
3 MOV R4, A
```

 


Figure 18: Simulation Waveform

It is possible to see in figure 18 that the value 10H is being stored on the accumulator, after the accumulator is subtracted by 20h which will result in a negative result, setting the carry bit of the PSW. Finally, the value on the accumulator is stored on the register R4.

5.1.3 ORL A, immediate

The following assembly code was tested.

```

1  MOV R2, #36h
2  MOV 53h, R2
3  MOV A, 53h
4  ORL A, #C9h

```

 


Figure 19: Simulation Waveform

It is possible to see in figure 19 that the value 32H is being stored on the register R2, next the value from value is stored on position 53H on the RAM, after the accumulator is loaded with the value from 53H and an OR is made with C9H resulting in FFH.

5.1.4 ANL A, immediate

The following assembly code was tested.

```

1 MOV R3, #36h
2 MOV 60h, R3
3 MOV A, 60h
4 ANL A, #C9h

```

 


Figure 20: Simulation Waveform

It is possible to see in figure 20 that the value 36H is being stored on the register R3, next the value from value is stored on position 60H on the RAM, after the accumulator is loaded with the value from 60H and an AND is made with C9H resulting in 00H.

5.1.5 XRL A, immediate

The following assembly code was tested.

```

1 MOV A, #10h
2 XRL A, #81h

```

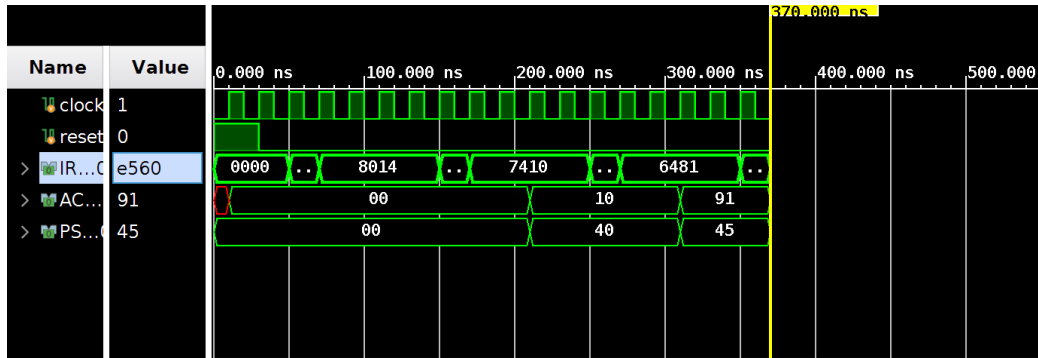


Figure 21: Simulation Waveform

It is possible to see in figure 21 that the value 19H is being loaded to the accumulator and next a XOR operation is made with 81H resulting in 91H.

5.2 Branch Instructions

5.2.1 JNC

The following assembly code was tested.

```

1 MOV A, #FFh
2 ADD A, #01h
3 JNC #02h
4 SUBB A, #FFh
5 MOV R7, A

```

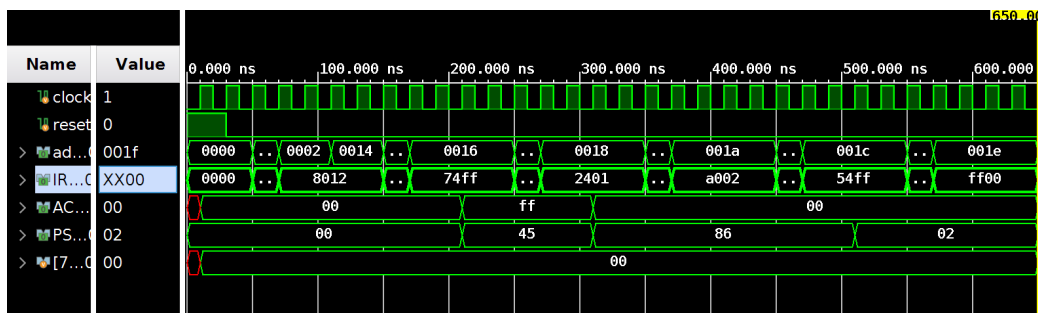


Figure 22: Simulation Waveform

It is possible to see in figure 22 that the first instruction to be executed is a SJMP with offset 12H, next is added 01H to FFH resulting in the carry bit being set which means that JNC would not jump, thus subtracting FFH to the accumulator and storing that value in the register R7.

The following assembly code was also tested.

```

1  MOV A, #FFh
2  ADD A, #00h
3  JNC #02h
4  SUBB A, #FFh
5  MOV R7, A

```

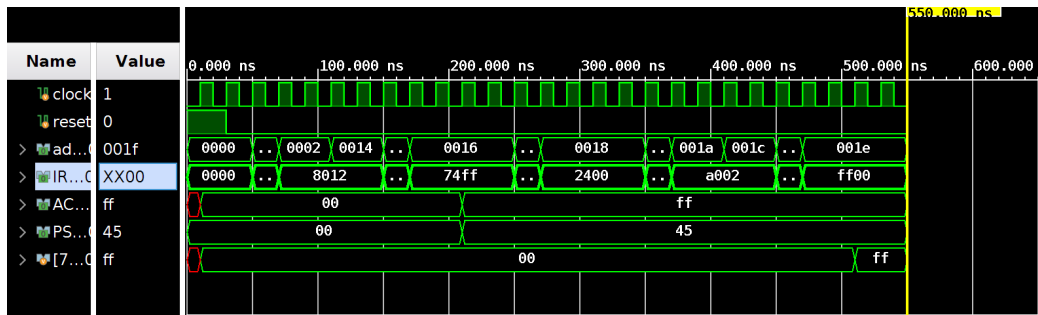


Figure 23: Simulation Waveform

It is possible to see in figure 23 that the first instruction to be executed is a SJMP with offset 12H, next is added 00H to FFH resulting in the carry bit being 0 which means that the jump with offset 02H did occur, thus not subtracting FFH to the accumulator and storing that value in the register R7.

5.2.2 JNZ

The following assembly code was tested.

```

1  MOV A, #08h
2  SUBB A, #09h
3  JNZ #02h
4  ADD A, #03h

```

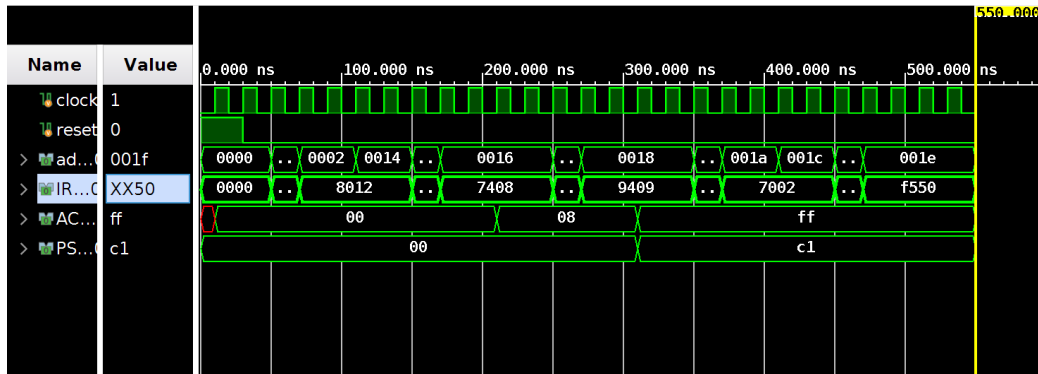


Figure 24: Simulation Waveform

It is possible to see in figure 24 that the first instruction to be executed is a SJMP with offset 12H, next the accumulator is loaded with 08H and subtracted 09H to its contents resulting in FFH, different than 0, which means JNZ would jump, thus not adding 03H to the accumulator.

The following assembly code was also tested.

```

1 MOV A, #08h
2 SUBB A, #08h
3 JNZ #02h
4 ADD A, #03h

```

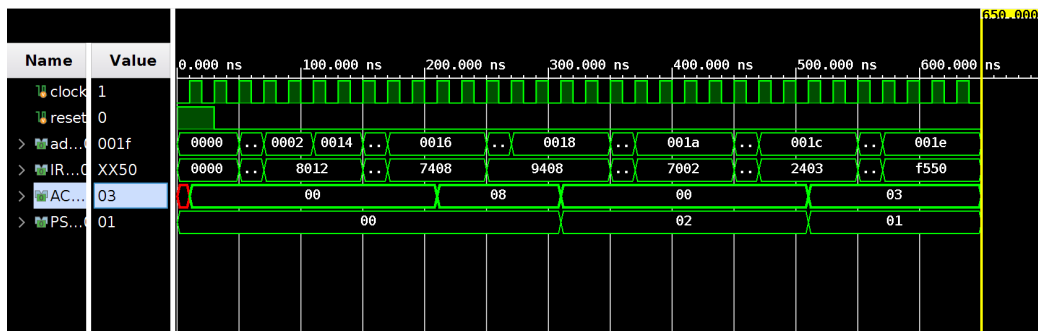


Figure 25: Simulation Waveform

It is possible to see in figure 25 that the first instruction to be executed is a SJMP with offset 12H, next, the accumulator is loaded with 08H and 08H is subtracted to its contents resulting in the result being 0 which means that the jump with offset 02H did not occur, thus adding 03H to the accumulator.

5.2.3 JZ

The following assembly code was tested.

```

1 MOV A, #08h
2 SUBB A, #08h
3 JNZ #02h
4 ADD A, #03h

```

 


Figure 26: Simulation Waveform

It is possible to see in figure 26 that the first instruction to be executed is a SJMP with offset 12H, next the accumulator is loaded with 08H and subtracted 08H to its contents resulting in 0, which means JZ would jump, thus not adding 03H to the accumulator.

The following assembly code was also tested.

```

1 MOV A, #08h
2 SUBB A, #09h
3 JNZ #02h
4 ADD A, #03h

```

It is possible to see in figure 27 that the first instruction to be executed is a SJMP with offset 12H, next, the accumulator is loaded with 08H and 09H is subtracted to its contents resulting in the result being FFH, which means that the jump with offset 02H did not occur, thus adding 03H to the accumulator.

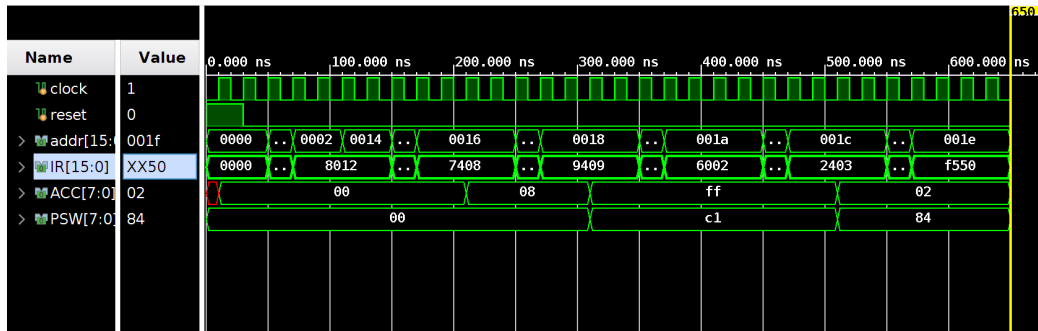


Figure 27: Simulation Waveform

5.3 Timer 0

5.3.1 Mode 1 - 16-bit timer

The Timer was loaded with the value FFF0h. In figure 28 it is possible to observe that the timer was loaded with FFF0h and when FFFFh was reached the overflow flag was set and the timer continue counting from 00h.

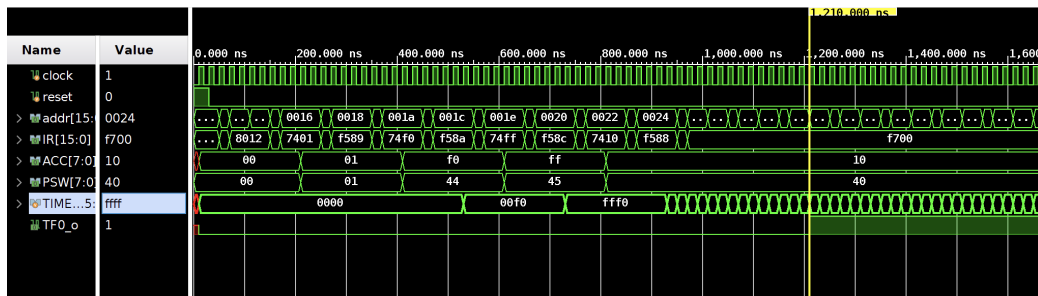


Figure 28: Simulation Waveform

5.3.2 Mode 2 - 8-bit auto reload timer

The Timer was loaded with the value F0h and the auto reload value was also set to F0h. In figure 29 it is possible to observe that the timer was loaded with F0h and when FFh was reached the overflow flag was set and the timer was reloaded with F0h counting.

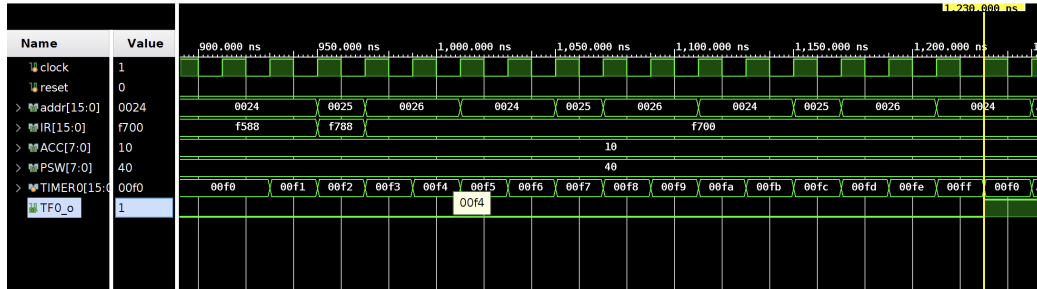


Figure 29: Simulation Waveform

5.4 Interrupts

5.4.1 Timer 0

The Timer 0 was loaded with 0000h and is operating in mode 1. In figure 30 it is possible to see that when the timer reached FFFFh both the overflow flag was set and the ISR_req signal were set and when the previous instruction finished executing the program counter was pushed to the stack before being updated with the Timer 0 ISR vector.

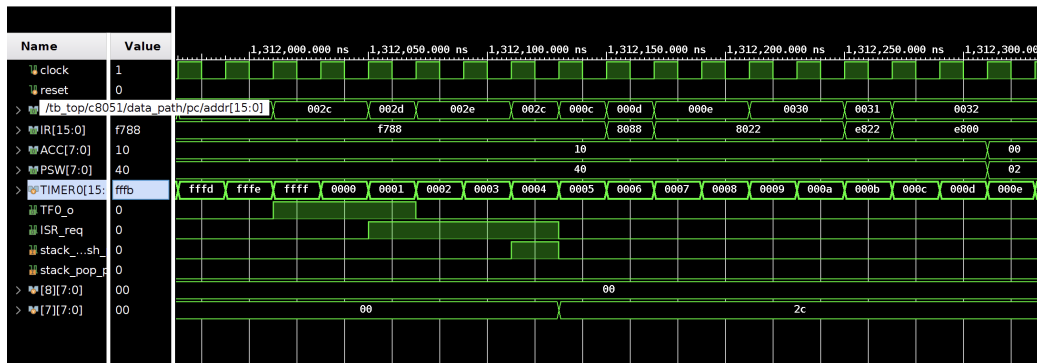


Figure 30: Simulation Waveform

5.4.2 External Interrupt 0

In figure 31, when the button (EI0_i) is pressed an interrupt request is launched and the program counter (addr) is pushed to the stack before being updated with the External Interrupt 0 ISR vector.

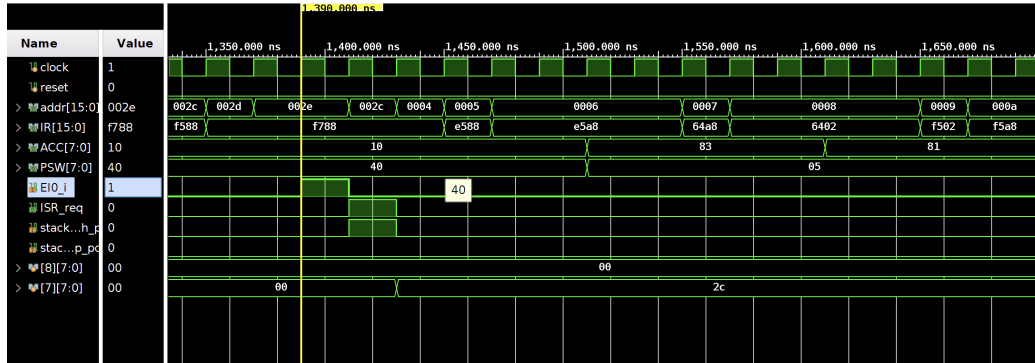


Figure 31: Simulation Waveform

5.5 Test in Hardware

The following code was run on the zybo and increments the I/O port P1 every second, this increment can be stopped or continue via an external interrupt.

In order to achieve this, the Timer 0 was configure in mode 1 - 16-bit timer and the registers TH0 and TL0 are loaded with 0, this would create a interrupt every 1.3ms so, to increment the output every second two registers are used, R0 that counts 255 interrupts and R1 that counts the number of times R0 overflows. When R1 reaches 3 the output is incremented. An external interrupt was also implemented in order to disable or enable the Timer 0 interrupt by switching the second bit of IE.

```

1      SJMP MAIN
2
3  EXT0:
4      MOV A, IE
5      XRL A, #02h
6      MOV IE, A
7      RETI
8
9  TIMER0:
10     SJMP TIMER0_ISR
11
12  MAIN:
13     MOV A, #01h
14     MOV TMOD, A
15     MOV A, #00h
16     MOV TL0, A

```

```
17     MOV TH0, A
18     MOV R0, #00h
19     MOV R1, #00h
20     MOV A, #83h
21     MOV IE, A
22     MOV A, #10h
23     MOV TCON, A
24     JNZ $
25
26 TIMER0_ISR:
27     MOV A, R0
28     ADD A, #01h
29     MOV R0, A
30     JNZ #12h
31     MOV A, R1
32     ADD A, #01h
33     MOV R1, A
34     SUBB A, #04h
35     JNZ #08h
36     MOV R1, #00h
37     MOV A, P1
38     ADD A, #01h
39     MOV P1, A
40     RETI
41
42 END
```

A video demonstrating this program working on the zybo can be found at <https://drive.google.com/file/d/1sjSU9oal2vwPEFB0H7fA2N8hXlndd8Kk/view?usp=sharing>

A Verilog module code

A.1 Datapath

```
1 module datapath(
2     input clock,
3     input reset,
4     input [7:0] ram_rd_byte, // byte read from RAM
5     input [7:0] rom_byte,    // byte read from ROM,
6     // connected to the input of the Instruction Register
7     input ram_rd_en_reg,     // Control signal that enables
8     // reading from RAM register bank
9     input ram_wr_en_reg,     // Control signal that enables
10    // writing to RAM register bank
11    input ram_rd_en_data,     // Control signal that enables
12    // reading from RAM data section
13    input ram_wr_en_data,     // Control signal that enables
14    // writing to RAM data section
15    input pc_inc,             // When this signal is high the
16    // program counter is incremented
17    input pc_set,             // When this signal is high the
18    // value on jmp_addr is added to the program counter
19    input pc_isr,             // When this signal is high the
20    // program counter is set to the isr vector present in
21    jmp_addr
22    input ir_load_high,       // When this signal is high the
23    // most significant byte of the IR is loaded with the byte
24    // fetched from ROM
25    input ir_load_low,        // When this signal is high the
26    // least significant byte of the IR is loaded with the byte
27    // fetched from ROM
28    input acc_load,           // Control signal to load the
29    // accumulator, connected to the accumulator write_en
30    input stack_pop_pc,       // Control signal to pop the
31    // program counter from the stack when the RETI instruction
32    // is executed
33    input ISR_req,            // Control signal to indicate
34    // that a interrupt needs to be serviced
35    input [7:0] ISR_v,        // ISR address vector provided
36    // to the program counter when an interrupt is triggered
37    input wire [15:0] jmp_addr_i, // Contains the program
38    // counter stored in the stack when the RETI instruction is
39    // executed
40    input psw_load,           // Control signal to load the
41    // PSW register
42    output wire [7:0] ram_rd_addr, // Address to read from
```

```

RAM
24   output wire [7:0] ram_wr_addr, // Address to write to
RAM
25   output wire [7:0] ram_wr_byte, // Byte to write to RAM
26   output [7:0] opcode,           // Instruction opcode
27   output wire [15:0] rom_addr,    // Program Counter output
   used to fetch instructions from ROM
28   output wire [7:0] psw_out       // Output of PSW
29   );
30
31
32   wire [15:0] pc_jump_addr;        // Jump address provided
   to the program counter
33   wire [15:0] IR;                 // Connected to the output
   of the Instruction Register
34   wire [7:0] alu_out;              // Result from the ALU
35   wire [7:0] acc_out;              // Output from ACC passed
   to the ALU as operand1
36   wire [7:0] register_b;           // Passed to the ALU as
   the second operand
37
38   wire psw_c;                     //carry bit
39   wire psw_ac;                    //auxiliary carry bit
40   wire psw_ov;                    //overflow bit
41   wire psw_z;                     //zero bit
42   wire psw_p;                     //parity bit
43
44   //Instanciation of the program counter module
45   program_counter pc(clock, reset, pc_inc, pc_set, pc_isr,
   pc_jump_addr, rom_addr);
46
47   //Instanciation of the instruction register module
48   instruction_register ir(clock, reset, ir_load_high,
   ir_load_low, rom_byte, IR);
49
50   //Instanciation of the ALU module
51   arithmetic_logic_unit alu(reset, acc_out, register_b, opcode
   [7:0], psw_out, alu_out, psw_c, psw_ac, psw_ov, psw_p, psw_z);
52
53   //Instanciation of the accumulator module
54   acc acc(clock, reset, alu_out, acc_load, acc_out);
55
56   //Instanciation of the PSW module
57   psw psw(clock, reset, psw_c, psw_ac, psw_ov, psw_z, psw_p
   , psw_load, psw_out);
58
59
60   assign opcode = IR[15:8]; // Assigning the opcode to the
   most significant byte of IR

```

```

61
62
63     assign ram_rd_addr = (ram_rd_en_data == 1'b1) ? IR[7:0] :
      8'hzz; //When ram_rd_en_data is high the address to read
      from the RAM is the least significant byte of IR
64     assign ram_wr_addr = (ram_wr_en_data == 1'b1) ? IR[7:0] :
      8'hzz; //When ram_wr_en_data is high the address to write
      to the RAM is the least significant byte of IR
65     assign register_b = (ram_rd_en_reg == 1'b1 ||
      ram_rd_en_data == 1'b1) ? ram_rd_byte : IR[7:0]; // If the
      second operand of the alu is fetched from RAM the byte
      read from RAM is passed to the ALU, else the least
      significant byte of the IR is passed as second operand
66     assign pc_jump_addr = (pc_set == 1'b1 && pc_isr == 1'b0) ?
      IR[7:0] : (pc_isr == 1'b1 && ISR_req == 1'b1) ? ISR_v : (
      stack_pop_pc == 1'b1) ? jmp_addr_i : 8'hzz; // The jump
      address can be provided by the IR in the form of an offset
      , as an isr vector or as the return address of isr
67     assign ram_wr_byte = (ram_wr_en_reg == 1'b1 && IR[15] ==
      0) ? IR[7:0] : acc_out; //If a register is being loaded
      with an immediate then the byte to write to the ROM is the
      least significant byte from IR, else, every other
      instruction writes the accumulator to the RAM
68
69 endmodule

```

A.1.1 Program counter

```

1 module program_counter(
2     input clock,
3     input reset,
4     input inc,           // When this signal is high the
      program counter is incremented
5     input set,           // When this signal is high the
      value on jmp_addr is added to the program counter
6     input isr,           // When this signal is high the
      program counter is set to the isr vector present in
      jmp_addr
7     input [15:0] jmp_addr, // Value for the program counter
      to be set
8     output reg [15:0] addr // Value of the program counter
9 );
10
11
12 initial begin
13     addr = 0;
14 end
15

```



```
16     always @(posedge clock) begin
17         if (reset) begin                //If the reset
signal is high the program counter is set to 0
18             addr <= 0;
19         end
20         else if(set==1 && isr==0) begin    //If set is high
the value on jmp_addr is added to the program counter
21             addr <= addr + jmp_addr;
22         end
23         else if(inc) begin                //If inc is high
the program counter is incremented
24             addr <= addr + 1;
25         end
26         else if(isr==1 && set==0) begin    //If isr is high
the program counter is set to the jmp_addr wich is
provided by the interrupt controller as the corresponding
isr vector
27             addr <= jmp_addr;
28         end
29     end
30
31 endmodule
```

A.1.2 Instruction Register

```
1 module instruction_register(
2     input clock,
3     input reset,
4     input ir_load_high,    //When this signal is high the
most significant byte of the IR is loaded with the byte
fetched from ROM
5     input ir_load_low,    //When this signal is high the
least significant byte of the IR is loaded with the byte
fetched from ROM
6     input [7:0] rom_byte,  //Byte fetched from ROM
7     output reg [15:0] IR   //Stores the instruction to be
executed
8 );
9
10 initial begin
11     IR = 0;
12 end
13
14 always @(posedge clock)
15 begin
16     if(reset)                //When reset is high the IR is
set to 0
17     begin
```

```
18         IR <= 0;
19     end
20     else if(ir_load_high) //The most significant byte of
IR is loaded with the rom byte
21     begin
22         IR[15:8] <= rom_byte;
23     end
24     else if (ir_load_low) //The least significant byte
of IR is loaded with the rom byte
25     begin
26         IR[7:0] <= rom_byte;
27     end
28 end
29
30 endmodule
```

A.1.3 Accumulator

```
1 module acc(
2     input clk,
3     input rst,
4     input [7:0] data_in, //data to be stored in the
accumulator
5     input write_en, //When this signal is high
data_in is stored in the ACC register
6     output reg [7:0] ACC //ACC register
7 );
8
9     always @(posedge clk) begin
10         if(rst) //When reset is high the
accumulator is set to 0
11         begin
12             ACC <= 0;
13         end
14
15         if (write_en) //ACC is loaded with data_in when
write_en is high
16         begin
17             ACC <= data_in;
18         end
19     end
20
21 endmodule
```

A.1.4 Program Status Word

```

1  /*
2  -----
3  |  CY  |  AC  |  FO  |  RS1  |  RS0  |  OV  |  Z  |  P  |
4  psw.7  psw.6  psw.5  psw.4  psw.3  psw.2  psw.1  psw.0 */
5
6
7  module psw(
8      input clk,
9      input rst,
10     input c,           //carry bit provided by the ALU
11     input ac,          //auxiliary carry bit provided by the
12                         ALU
13     input ov,          //overflow bit provided by the ALU
14     input z,           //zero bit provided by the ALU
15     input p,           //parity bit provided by the ALU (
16                         high -> odd)
17     input write_en,     //When high the PSW is updated with
18                         the bits provided above
19     output reg [7:0] PSW //PSW register
20 );
21
22
23     initial begin
24         PSW = 8'b00000000;
25     end
26
27     always @(posedge clk) begin
28         if(rst)           //When reset is high the PSW
29                         is set to 0
30         begin
31             PSW <= 8'b00000000;
32         end
33
34         if (write_en)     //When write_en is high the PSW
35                         is updated with the status bits
36         begin
37             PSW[7] <= c;
38             PSW[6] <= ac;
39             PSW[2] <= ov;
40             PSW[1] <= z;
41             PSW[0] <= p;
42         end
43     end
44 endmodule

```

A.1.5 Arithmetic Logic Unit

```

1 module arithmetic_logic_unit(
2     input reset,
3     input [7:0] operand1,    //First operand connected to the
                                //output of the accumulator, as all operations implemented
                                //use the accumulator as source operand
4     input [7:0] operand2,    //Second operand
5     input [7:0] opcode,      //Instruction opcode
6     input [7:0] PSW,         //PSW register
7     output [7:0] result_o,   //Result from operation
8     output psw_c,            //carry bit
9     output psw_ac,           //auxiliary carry bit
10    output psw_ov,           //overflow bit
11    output psw_p,            //parity bit
12    output psw_z              //zero bit
13 );
14
15
16 `include "opcodes.v"
17
18 reg [8:0] result; //register to store the result of the
                    //operation, the ninth bit is used to store the carry bit
19
20 initial begin
21     result = 9'b000000000;
22 end
23
24 assign result_o = result[7:0]; //assign the 8 least
                                //significant bits of the result to result_o
25
26 assign psw_c = result[8]; //The carry bit is assigned
                            //the value of the ninth bit of the result of an arithmetic
                            //operation.
27 assign psw_ac = result[4]; //The auxiliary carry is set
                            //when there's a carry from bit 3 to bit 4 of the result
28 assign psw_ov = result[8]&&~result[7] || result[7]&&~
                            //result[8]; //The overflow bit is set when the result is
                            //higher than 128 or smaller than -128
29 assign psw_p = result[7:0]%2; //The parity bit is set
                                //when the result is odd
30 assign psw_z = ~(result[7] | result[6] | result[5] |
                    //result[4] | result[3] | result[2] | result[1] | result[0])
                    //; //The zero bit is set when the result is zero
31
32
33
34 always @(*)
35     begin

```

```
36         if(reset)
37         begin
38             result = 9'b0000000000;
39         end
40         casex(opcode)
41
42             `MOV_AI : begin
43                 result[7:0] = operand2; //result is
connected to the input of the accumulator, accumulator is
loaded with the value from operand2
44             end
45             `MOV_AR : begin //result is connected to
the input of the accumulator, accumulator is loaded with
the value from operand2
46                 result[7:0] = operand2;
47             end
48             `MOV_AD: begin
49                 result[7:0] = operand2;
50             end
51             `ADD : begin
52                 result = operand1 + operand2;
53             end
54             `SUBB : begin
55                 result = operand1 - operand2;
56             end
57             `ANL: begin
58                 result = operand1 & operand2;
59             end
60             `ORL:begin
61                 result = operand1 | operand2;
62             end
63             `XRL:begin
64                 result = operand1 ^ operand2;
65             end
66             default:
67                 result=result;
68         endcase
69     end
70 endmodule
```

A.2 Control Unit

```
1 module control_unit(
2     input clock,
3     input reset,
4     input [7:0] opcode,           //Instruction opcode
```

```

5      input ISR_req,                //Control signal is high
when a interrupt needs to be serviced
6      input [7:0] PSW,              //PSW register
7      output ram_rd_en_reg,         // Control signal that
enables reading from RAM register bank
8      output ram_wr_en_reg,         // Control signal that
enables writing to RAM register bank
9      output [2:0] ram_reg_in_sel,  // Selection signal for
register to write to
10     output [2:0] ram_reg_out_sel,  // Selection signal for
register to read from
11     output ram_rd_en_data,         // Control signal that
enables reading from RAM data section
12     output ram_wr_en_data,         // Control signal that
enables writing to RAM data section
13     output rom_en,                // Control signal to
fetch byte from ROM
14     output pc_inc,                // When this signal is
high the program counter is incremented
15     output pc_set,                // When this signal is
high the value on pc_jump_addr is added to the program
counter
16     output pc_isr,                // When this signal is
high the program counter is set to the isr vector present
in pc_jump_addr
17     output ir_load_high,          // When this signal is
high the most significant byte of the IR is loaded with
the byte fetched from ROM
18     output ir_load_low,           // When this signal is
high the least significant byte of the IR is loaded with
the byte fetched from ROM
19     output acc_load,              // Control signal to load
the accumulator
20     output stack_push_pc,         // Control signal to push
the program counter to the stack when the interrupt is
served
21     output stack_pop_pc,          // Control signal to pop
the program counter from the stack when the RETI
instruction is executed
22     output psw_load               // Control signal to load
the PSW
23 );
24
25 `include "opcodes.v"
26
27
28 reg [4:0] state;
29
30 //===== Internal Constants =====

```

```

31  parameter s_start    = 5'b00000,
32          s_fetch_1 = 5'b00001,      //state to fetch the
    most significant byte of the instruction to be executed
33          s_fetch_2 = 5'b00010,      //state to fetch the
    least significant byte of the instruction to be executed
34          s_decode  = 5'b00011,      //state to decode the
    opcode
35          s_mov_ri  = 5'b00100,      //state to execute
    the instruction to move an immediate to a register
36          s_mov_ai  = 5'b00101,      //state to execute
    the instruction to move an immediate to the accumulator
37          s_mov_ar  = 5'b00110,      //state to execute
    the instruction to move the value on register to
    accumulator
38          s_add_ai  = 5'b00111,      //state to execute
    the instruction to add an immediate with the accumulator
39          s_mov_ra  = 5'b01000,      //state to execute
    the instruction to move the value on the accumulator to a
    register
40          s_subb_ai = 5'b01001,      //state to execute
    the instruction to subtract an immediate with the
    accumulator
41          s_orl_ai  = 5'b01011,      //state to execute
    the instruction to or an immediate with the accumulator
42          s_andl_ai = 5'b01101,      //state to execute
    the instruction to and an immediate with the accumulator
43          s_xrl_ai  = 5'b01111,      //state to execute
    the instruction to xor an immediate with the accumulator
44          s_jnz     = 5'b10001,      //state to execute
    the jump if not zero instruction
45          s_jz      = 5'b10010,      //state to execute
    the jump if zero instruction
46          s_sjmp    = 5'b10011,      //state to execute
    the short jump instruction
47          s_jnc     = 5'b10100,      //state to execute
    the jump if carry is zero instruction
48          s_mov_ad  = 5'b10101,      //state to execute
    the instruction to move a direct to the accumulator
49          s_mov_dr  = 5'b10110,      //state to execute
    the instruction to move a register to a direct
50          s_ret     = 5'b10111,      //state to execute
    the instruction to return from isr routine
51          s_mov_da  = 5'b11000,      //state to execute
    the instruction to move the accumulator to a direct
52          s_halt    = 5'b11111;
53  //=====
54
55
56  initial begin

```

```

57     state <= s_start;
58 end
59
60 assign rom_en = (state == s_fetch_1 || state == s_fetch_2) ?
    1'b1 : 1'b0;
61 assign pc_inc = (state == s_fetch_1 || state == s_fetch_2) ?
    1'b1 : 1'b0;
62
63 assign ir_load_high = (state == s_fetch_1) ? 1'b1 : 1'b0;
64 assign ir_load_low = (state == s_fetch_2) ? 1'b1 : 1'b0;
65
66 assign ram_wr_en_reg = (state == s_mov_ri || state ==
    s_mov_ra) ? 1'b1 : 1'b0;
67 assign ram_reg_in_sel = (state == s_mov_ri || state ==
    s_mov_ra) ? opcode[2:0] : 3'bzzz;
68
69 assign ram_rd_en_reg = (state == s_mov_ar || state ==
    s_mov_dr) ? 1'b1 : 1'b0;
70 assign ram_reg_out_sel = (state == s_mov_ar || state ==
    s_mov_dr) ? opcode[2:0] : 3'bzzz;
71 assign ram_rd_en_data = (state == s_mov_ad) ? 1'b1 : 1'b0;
72 assign ram_wr_en_data = (state == s_mov_dr || state ==
    s_mov_da) ? 1'b1 : 1'b0;
73
74 assign acc_load = (state == s_xrl_ai || state == s_orl_ai ||
    state == s_andl_ai || state == s_subb_ai || state ==
    s_mov_ai || state == s_mov_ad || state == s_mov_ar ||
    state == s_add_ai) ? 1'b1 : 1'b0;
75
76 assign pc_set = ((state == s_sjmp) || (state == s_jnz && ~PSW
    [1]) || (state == s_jz && PSW[1]) || (state == s_jnc && ~
    PSW[7]) || state == s_halt ) ? 1'b1 : 1'b0;
77
78 // The interrupt is serviced when the current instruction
    finishes execution
79 assign pc_isr = ((state == s_start && ISR_req == 1'b1) ||
    state == s_reti || state == s_halt) ? 1'b1 : 1'b0;
80
81 assign stack_push_pc = (state == s_start && ISR_req) ? 1'b1 :
    1'b0;
82
83 assign stack_pop_pc = (state == s_reti) ? 1'b1 : 1'b0;
84
85 assign psw_load = acc_load;
86
87 always @ (posedge clock)
88
89 begin : FSM
90     if (reset == 1'b1) begin // reset

```



```

91     state <= s_start;
92 end
93 else begin
94     case(state)
95         s_start :
96             if(reset != 1'b1)
97                 begin
98                     state <= s_fetch_1;
99                 end
100
101     s_fetch_1:
102         state <= s_fetch_2;
103     s_fetch_2:
104         state <= s_decode;
105     s_decode :
106         casex(opcode)
107             `MOV_RI:
108                 state <= s_mov_ri;
109             `MOV_DR:
110                 state <= s_mov_dr;
111             `MOV_AD:
112                 state <= s_mov_ad;
113             `MOV_RA:
114                 state <= s_mov_ra;
115             `SJMP:
116                 state <= s_sjmp;
117             `MOV_AI:
118                 state <= s_mov_ai;
119             `MOV_AR:
120                 state <= s_mov_ar;
121             `MOV_DA:
122                 state <= s_mov_da;
123             `ADD_AI:
124                 state <= s_add_ai;
125             `SUBB_AI:
126                 state <= s_subb_ai;
127             `ORL_AI:
128                 state <= s_orl_ai;
129             `ANL_AI:
130                 state <= s_anl_ai;
131             `XRL_AI:
132                 state <= s_xrl_ai;
133             `JNZ:
134                 state <= s_jnz;
135             `JZ:
136                 state <= s_jz;
137             `JNC:
138                 state <= s_jnc;
139             `RETI:

```

```
140         state <= s_ret;
141     `HALT:
142         state <= s_halt;
143     default :
144         state <= s_fetch_1;
145     endcase
146 s_mov_ri:
147     state <= s_start;
148 s_mov_ai:
149     state <= s_start;
150 s_mov_ad:
151     state <= s_start;
152 s_mov_dr:
153     state <= s_start;
154 s_mov_ar:
155     state <= s_start;
156 s_mov_da:
157     state <= s_start;
158 s_add_ai:
159     state <= s_start;
160 s_mov_ra:
161     state <= s_start;
162 s_subb_ai:
163     state <= s_start;
164 s_orl_ai:
165     state <= s_start;
166 s_andl_ai:
167     state <= s_start;
168 s_xrl_ai:
169     state <= s_start;
170 s_jnz:
171     state <= s_start;
172 s_jz:
173     state <= s_start;
174 s_sjmp:
175     state <= s_start;
176 s_jnc:
177     state <= s_start;
178 s_ret:
179     state <= s_start;
180 s_halt:
181     state <= s_start;
182     default :
183         state <= s_start;
184 endcase
185 end
186 end
187
188 endmodule
```

A.3 RAM

```

1
2 module ram(
3     input clock,
4     input reset,
5     input ram_rd_en_reg,
6     input ram_wr_en_reg,
7     input [2:0] ram_reg_in_sel,
8     input [2:0] ram_reg_out_sel,
9     input ram_rd_en_data,
10    input ram_wr_en_data,
11    input [7:0] ram_rd_addr,
12    input [7:0] ram_wr_addr,
13    input [7:0] ram_wr_byte,
14    input stack_push_pc,
15    input stack_pop_pc,
16    input TF0_i,                //Overflow flag from
timer0
17    input [15:0] pc_reti_in,
18    output [7:0] ram_rd_byte,
19    output [7:0] tcon,          //Output the TCON register
20    output [7:0] tmod,         //Output the TMOD register
21    output [7:0] TL0,          //Output the TL0 register
22    output [7:0] TH0,          //Output the TH0 register
23    output [15:0] jmp_addr_o,  //Output for the return
address for the ISR
24    output [7:0] PORT1_o,      //Output for the I/O port
P1
25    output [7:0] IE_o          //Output the IE register
26 );
27
28
29 reg [7:0] mem [0:255];
30 integer i;
31 reg [7:0] SP;
32
33 //Instanciate the register bank
34 register_bank REG(clock,reset,ram_wr_en_reg,ram_rd_en_reg
,ram_reg_in_sel,ram_reg_out_sel,ram_wr_byte,ram_rd_byte);
35
36 assign tcon = mem[8'h88];    //TCON address: 0x88h
37 assign tmod = mem[8'h89];    //TMOD address: 0x89h
38 assign TL0  = mem[8'h8A];    //TL0  address: 0x8Ah
39 assign TH0  = mem[8'h8C];    //TH0  address: 0x8Ch
40 assign IE_o = mem[8'hA8];    //IE   address: 0xA8h
41 assign PORT1_o = mem[8'h90]; //P1   address: 0x90h
42
43 always @(posedge clock)

```

```

44     begin
45         if(reset)      //If reset is high clear RAM and set
stack pointer to address 0x07h
46         begin
47             for(i=0; i < 256 ; i = i + 1)
48                 begin
49                     mem[i]=8'b00000000;
50                 end
51             SP = 8'h07;
52         end
53
54         mem[8'h88][5] = TF0_i; //Update TCON with the Timer
0 overflow flag
55
56         if(ram_wr_en_data == 1'b1 && ram_rd_en_reg == 1'b0)
//Write to RAM data section
57         begin
58             mem[ram_wr_addr] = ram_wr_byte;
59         end
60         if(ram_wr_en_data == 1'b1 && ram_rd_en_reg == 1'b1)
//Write value read from register to address on RAM
61         begin
62             mem[ram_wr_addr] = ram_rd_byte;
63         end
64         if(stack_push_pc == 1'b1) //Push the program counter
to the stack when isr is going to be executed
65         begin
66             mem[SP] = pc_reti_in[7:0];
67             mem[SP+1] = pc_reti_in[15:8];
68             SP = SP+2;
69         end
70         else if (stack_pop_pc == 1'b1) //Pop the program
counter from the stack when returning from isr
71         begin
72             SP = SP - 2;
73         end
74     end
75
76     assign ram_rd_byte = (ram_rd_en_data == 1'b1 &&
ram_rd_en_reg == 1'b0 ) ? mem[ram_rd_addr] : 8'hzzz; //Read
the value from the data section of ram
77
78     assign jmp_addr_o = (stack_pop_pc == 1'b1) ? {mem[SP-1],
mem[SP-2]} : 16'hzzzz; //Read the program counter from
the stack
79
80 endmodule

```

A.4 ROM

```

1 module rom(
2     input reset,
3     input rom_en,          //Control signal to fetch byte
    from rom
4     input [15:0] rom_addr, //Address to fetch byte
5     output [7:0] rom_byte  //Output the byte fetched
6 );
7
8     reg [7:0] ROM[0:255];
9
10
11     always @(posedge reset) begin
12
13         //-----interrupt vectors-----
14
15         //reset
16         ROM[0]  = 8'b10000000;
17         ROM[1]  = 8'b00010010;
18
19         ROM[2]  = 8'b00100100;
20         ROM[3]  = 8'b00000001;
21         //External 0
22         ROM[4]  = 8'b00100100;
23         ROM[5]  = 8'b00000001;
24
25         ROM[6]  = 8'b11110101;
26         ROM[7]  = 8'b10010000;
27
28         ROM[8]  = 8'b00110010;
29         ROM[9]  = 8'b00000000;
30
31         ROM[10] = 8'b01110100;
32         ROM[11] = 8'b00000010;
33
34         //Timer 0
35         ROM[12] = 8'b10000000;
36         ROM[13] = 8'b00100010;
37
38         ROM[14] = 8'b11110101;
39         ROM[15] = 8'b10010000;
40
41         ROM[16] = 8'b00110010;
42         ROM[17] = 8'b00000000;
43
44         ROM[18] = 8'b00110010;
45         ROM[19] = 8'b00000000;
46         //-----

```

```

47 //-----code-----
48     ROM[20] = 8'b01110100; //MOV A, #01h
49     ROM[21] = 8'b00000001;
50
51     ROM[22] = 8'b11110101; //MOV TMOD, A
52     ROM[23] = 8'b10001001;
53
54     ROM[24] = 8'b01110100 ; //MOV A, #00h
55     ROM[25] = 8'b00000000;
56
57     ROM[26] = 8'b11110101; //MOV TLO, A
58     ROM[27] = 8'b10001010;
59
60     ROM[28] = 8'b01110100; //MOV A, #00h
61     ROM[29] = 8'b00000000;
62
63     ROM[30] = 8'b11110101; // MOV TH0, A
64     ROM[31] = 8'b10001100;
65
66     ROM[32] = 8'b01111000; //MOV R0, #00h
67     ROM[33] = 8'b00000000;
68
69     ROM[34] = 8'b01111001; // MOV R1, #00h
70     ROM[35] = 8'b00000000;
71
72     end
73
74     assign rom_byte = (rom_en == 1'b1) ? ROM[rom_addr] : 8'
75     hzz;
76 endmodule

```

A.5 Timer 0

```

1 module timer0(
2     input clock,
3     input reset,
4     input [7:0] tmod,    //TMOD register
5     input [7:0] tcon,    //TCON register
6     input [7:0] TH0_i,   //TH0 register
7     input [7:0] TL0_i,   //TL0 register
8     input TF0_clr,       //Control signal to clear the
9     overflow flag
10    output reg TF0_o      //Overflow flag
11);
12
13    reg [15:0] TIMER0;
14    reg [7:0] TH0;

```

```

14     reg [7:0] TL0;
15
16
17     always @(posedge clock)
18     begin
19         if(reset == 1'b1)
20         begin
21             TH0 = 8'h00;
22             TL0 = 8'h00;
23             TIMER0 = 0;
24             TFO_o = 0;
25         end
26         if(TF0_clr) begin
27             TFO_o = 0;
28         end
29         case(tmod[1:0])
30             2'b01: // Mode 1: 16 bit timer
31                 begin
32                     if(tcon[4] == 1'b0) begin // timer not
running
33                         TH0 = TH0_i;
34                         TL0 = TL0_i;
35                         TFO_o = 1'b0;
36                         TIMER0 = {TH0,TL0};
37                     end
38                     else if(tcon[4] == 1'b1) begin // timer
running
39                         TIMER0 = TIMER0 + 1;
40                     end
41                     if(TIMER0 == 16'hFFFF) begin //overflow
42                         TFO_o = 1'b1;
43                     end
44                 end
45
46             2'b10: //Mode 2: 8 bit timer with auto-reload
47                 begin
48                     if(tcon[4] == 1'b0) begin
49                         TH0 = TH0_i;
50                         TL0 = TL0_i;
51                         TFO_o = 1'b0;
52                         TIMER0 = {8'h00,TL0};
53                     end
54                     if(TIMER0[7:0] == 8'hFF)
55                     begin
56                         TFO_o = 1'b1;
57                         TIMER0 = {8'h00,TH0};
58                     end
59                     else if(tcon[4] == 1'b1) begin
60                         TIMER0 = TIMER0 + 1;

```

```
61         end
62     end
63     default:
64         TIMERO = 0;
65
66     endcase
67 end
68
69 endmodule
```

A.6 Interrupt Controller

```
1 module interrupt_controller(
2     input clock,
3     input reset,
4     input stack_push_pc,      //Control signal that
    indicates that the interrupt has been attended
5     input [7:0] IE_i,         //IE register
6     input [7:0] TCON_i,       //TCON register
7     input EIO_i,              //Button input for external
    interrupt
8     output TF0_clr,           //Control signal to clear
    Timer 0 overflow flag
9     output reg [7:0] ISR_v,    //ISR vector
10    output reg ISR_req          //Signal to indicate that
    there is an interrupt to be serviced
11 );
12
13    assign TF0_clr = (ISR_req == 1'b1) ? 1'b1 : 1'b0; //If
    the interrupt has been requested the timer overflow flag
    is automatically cleared
14
15    always @(posedge clock)
16    begin
17        if(reset)
18        begin
19            ISR_v = 0;
20            ISR_req = 0;
21        end
22        if(stack_push_pc) begin //If stack_push_pc is high
    it means that the interrupt request has been attended
23            ISR_req = 1'b0;
24        end
25        else if(EIO_i && IE_i[7] && IE_i[0] && !ISR_req) //
    External interrupt 0
26        begin
27            ISR_req = 1'b1;
28            ISR_v = 16'h0004;
```



```
29         end
30
31         else if (TCON_i[5] && IE_i[7] && IE_i[1] && !ISR_req)
32             //Timer 0 interrupt
33             begin
34                 ISR_req = 1'b1;
35                 ISR_v = 16'h000C;
36             end
37         end
38     endmodule
```